

IIT KHARAGPUR

SWITCHING CIRCUIT LABORATORY
CS29204

Assignment: 2

Group 01

Nikhil Saraswat (20CS10039)

Abhijeet Singh (20CS30001)

Gopal (20CS30021)

Rohit Kumar Prajapati (20CS30041)



Problem 1 (BCD)

Problem Statement: -

- Develop circuits to convert from 4-bit binary to 2-digit BCD.

Description of the Solution including Logic Expression: -

4-bit binary to 2-digit BCD

In this problem we have four inputs A, B, C and D. A represents the third bit of 4 bit binary, B represents the second bit of 4 bit binary, C represents first bit of 4 bit binary and D represents zeroth bit of 4 bit binary.

We have to convert it into 5-bit BCD but since BCD is usually of 8 bits so we are adding 3 buffer bits P, Q and R at the starting of output.

For S: The input at A and the input at B is passed through a common AND gate and also the input add A and the input at C is passed through a common AND gate. The output provided by these two AND gates is then passed through a OR gate to obtain final output at S which is the fourth bit of BCD.

Output at $S = AB + AC$

For T: The input provided at B and C is passed through a NOT gate which is then combined at an AND gate with the input provided at A. The output of this AND gate is the final output of T which is the third bit of BCD.

Output at $T = AB'C'$

For U: The output obtained by passing input of A through NOT gate and input provided at B is combined by an AND gate. Another AND gate combines the input provided at B and C. The output of the above two AND gates is passed through a OR gate and the output obtained through this is the final output obtained at U.

Output at $U = A'B + BC$


For V: The input provided at A and B is combined with the output obtained by passing the input of C through NOT gate at an AND gate. At another AND gate input provided by C and output provided by passing by the input of A through NOT gate is combined. The output obtained by the above two AND gates is passed through a OR gate to obtain the final output of V which is the first bit of BCD.

Output at $V = ABC' + A'C$

For W: The input provided at D is the output at W which is zeroth bit of BCD.

Output at $W = D$

Circuit Diagram: -

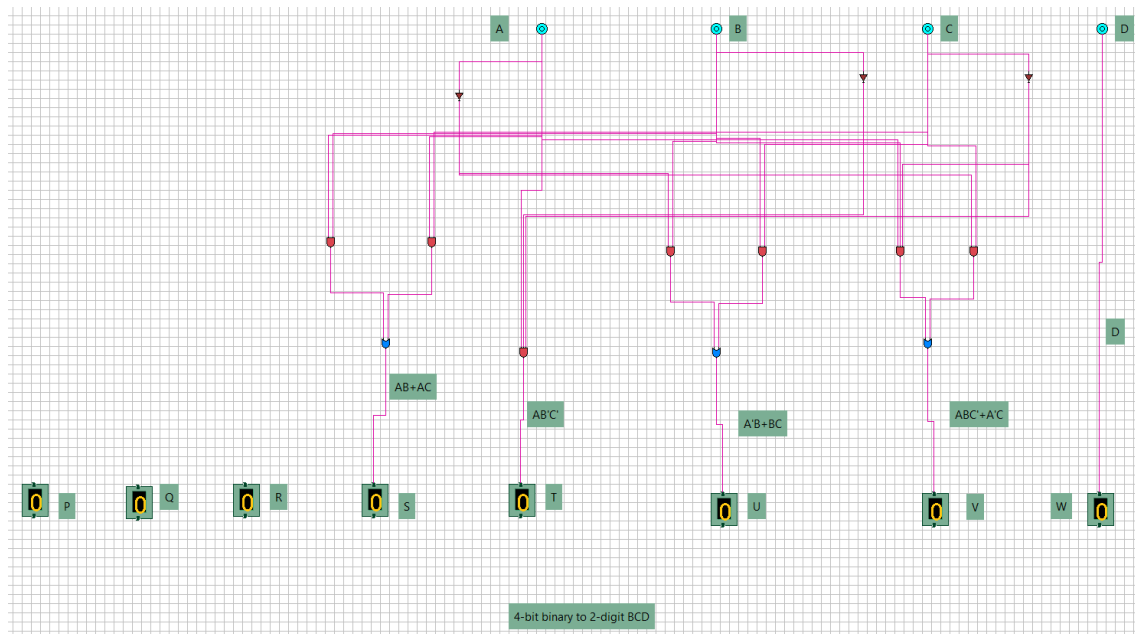

Problem 2 (Gray)

Problem Statement: -

- Develop circuits to convert from 4-bit Gray to 4-bit binary and vice-versa.

Description of the Solution including Logic Expression: -

4-bit Gray to 4-bit binary

For P: A represents the third bit of Gray and the input provided at A is the output obtained at P which is the third bit of binary.

Output at P = A

For Q: B represents the second bit of Gray. The input provided at A and the input provided at B is passed through XOR gate to obtain the final output at Q which is second bit of binary.

Output at Q = $A \oplus B$

For R: C represents the first bit of Gray. The input at A and the input at B is passed through XOR gate and the output then obtained and the input provided at C is again passed through a XOR gate. The output obtained through this XOR gate is the final output obtained at R which is the first bit of binary.

Output at R = $A \oplus B \oplus C$

For S: D is the zeroth bit of Gray. The output obtained at R and input provided at D is then passed through XOR gate to obtain the final output at S which is zeroth bit off binary.

Output at S = $A \oplus B \oplus C \oplus D$

4-bit binary to-bit Gray

For P: The input provided at A is the final output provided at P.

Output at P = A

For Q: The input provided at A and the input provided at B is passed through a XOR gate to obtain final output at Q.

Output at Q = $A \oplus B$


For R: Similarly, the input provided at B and the input provided at C is passed through a XOR gate to obtain the final output at R.


Output at R = $B \oplus C$

For S: Similarly, the input provided at C and the input provided at D is passed through a XOR gate to obtain the final output at S.

Output at S = $C \oplus D$

Circuit Diagram: -

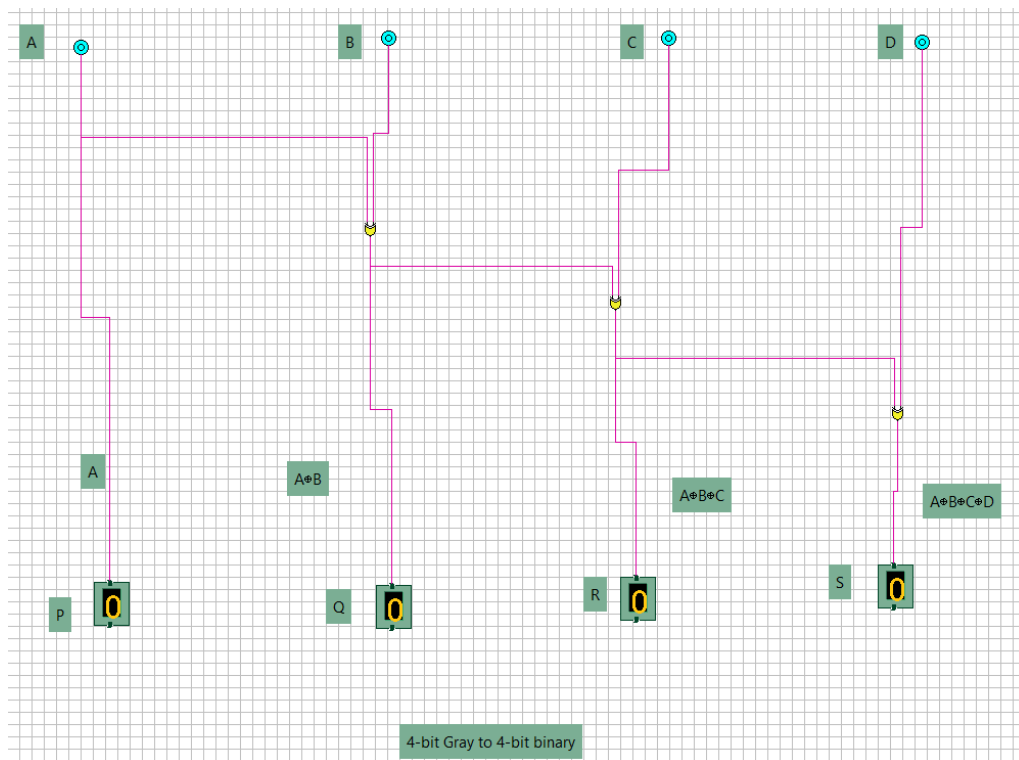

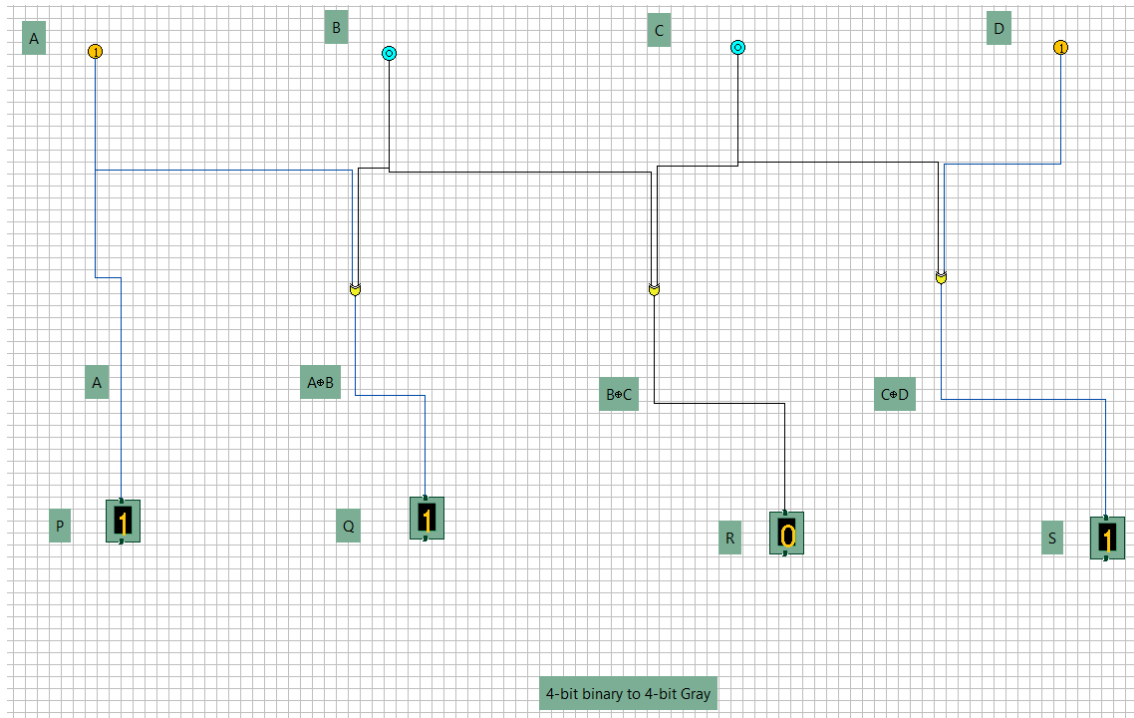

Problem 3 (Excess-3)

Problem Statement: -

- Develop a half adder for handling two bits.
- Develop a full adder using half adders and any additional logic.
- Develop a ripple carry adder needed for this assignment using full adders.
- Develop circuits to convert from excess-3 to 4-bit binary and vice-versa.

Description of the Solution including Logic Expression: -

Half Adder

Input -: A, B

Sum of the half adder is obtained by passing the inputs of A and B through XOR gate whereas carry of half adder is obtained by passing the inputs of A and B by AND gate.

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A.B$$

Full Adder

Inputs: - P, Q, Carry-in

Components Used: - Two half adders and an OR gate.

$$\text{Carry out} = P.Q + Q.C\text{-in} + P.C\text{-in}$$

$$\text{Sum} = (C\text{in}) \oplus (P \oplus Q)$$

Ripple Carry Adder

Inputs: - Two four-bit numbers and a carry-in.

Components Used: - 4 full adders.

Two numbers which are written in four-bit form along with Carry-in is taken as input. The carry-out obtained from the first full adder is used as carry-in for the second full adder and so on.

$$S_0 = A_0 \oplus B_0 \oplus C_{in}$$

$$S_1 = A_1 \oplus B_1 \oplus C_0$$

$$S_2 = A_2 \oplus B_2 \oplus C_1$$

$$S_3 = A_3 \oplus B_3 \oplus C_2$$

$$\text{Carry-out} = A_3 B_3 \oplus B_3 C_2 \oplus C_2 A_3$$

Excess-3 to 4-Bit Binary

Inputs: - W, X, Y, Z

Components Used: - 7 AND gates, 3 NOT gates, and 3 OR gates

$$\text{Output at A} = WX + WYZ$$

$$\text{Output at B} = X'Y' + X'Z' + XYZ$$

$$\text{Output at C} = Y \oplus Z$$

$$\text{Output at D} = Z'$$

Excess-3 to 4-Bit Binary

Inputs: - A, B, C and D

Components Used: - 4 AND gates, 3 NOT gates, and 4 OR gates



$$\text{Output at W} = A + BC + BD$$



$$\text{Output at X} = B'C + B'D + BC'D'$$

$$\text{Output at Y} = CD + C'D'$$

$$\text{Output at Z} = D'$$

Circuit Diagram: -

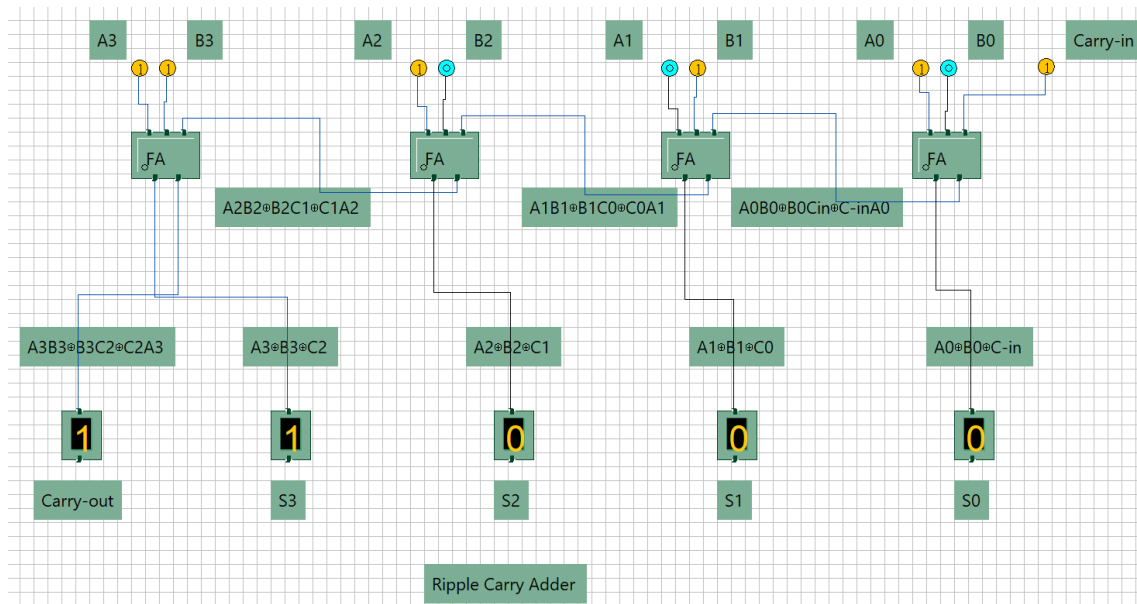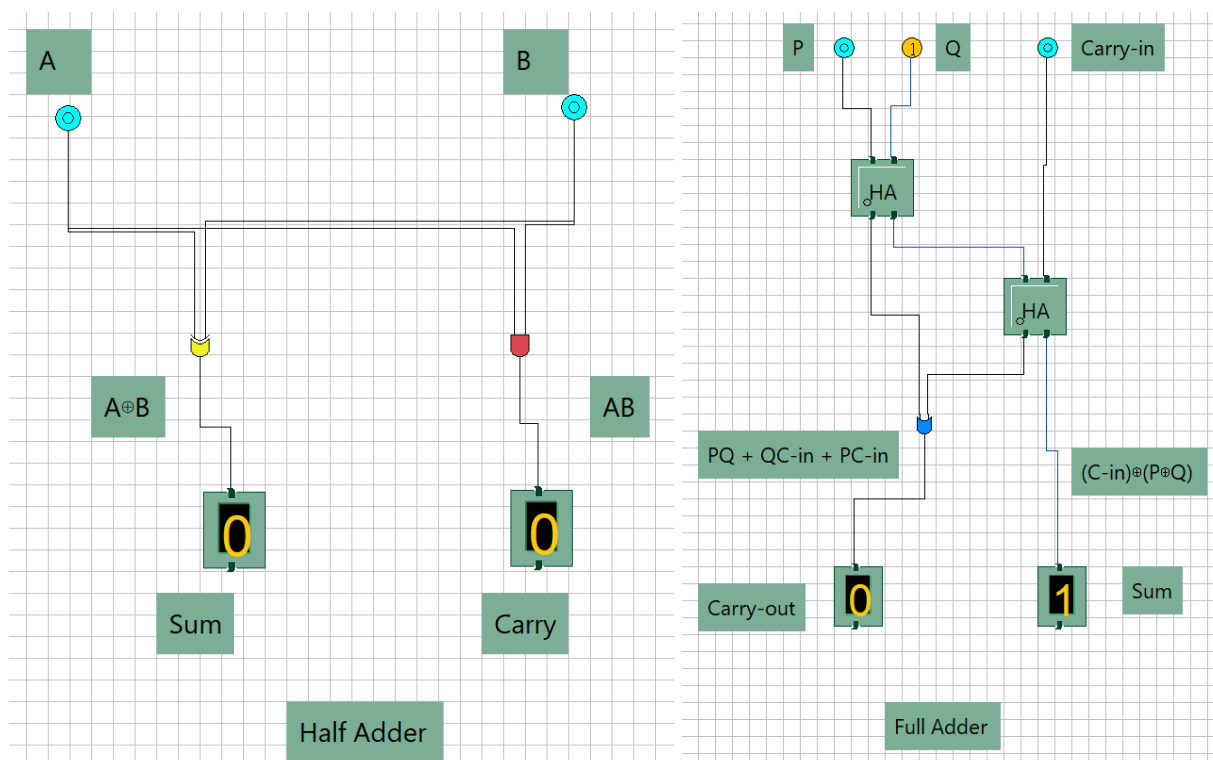

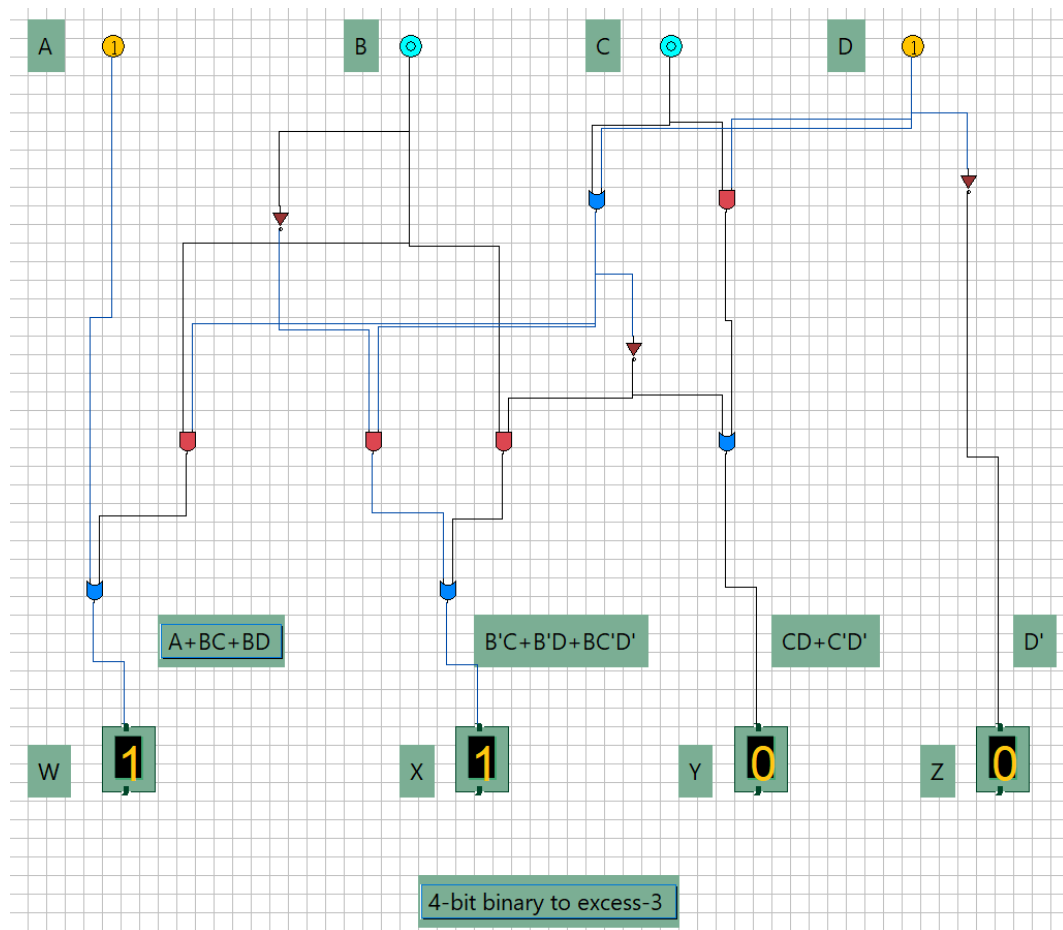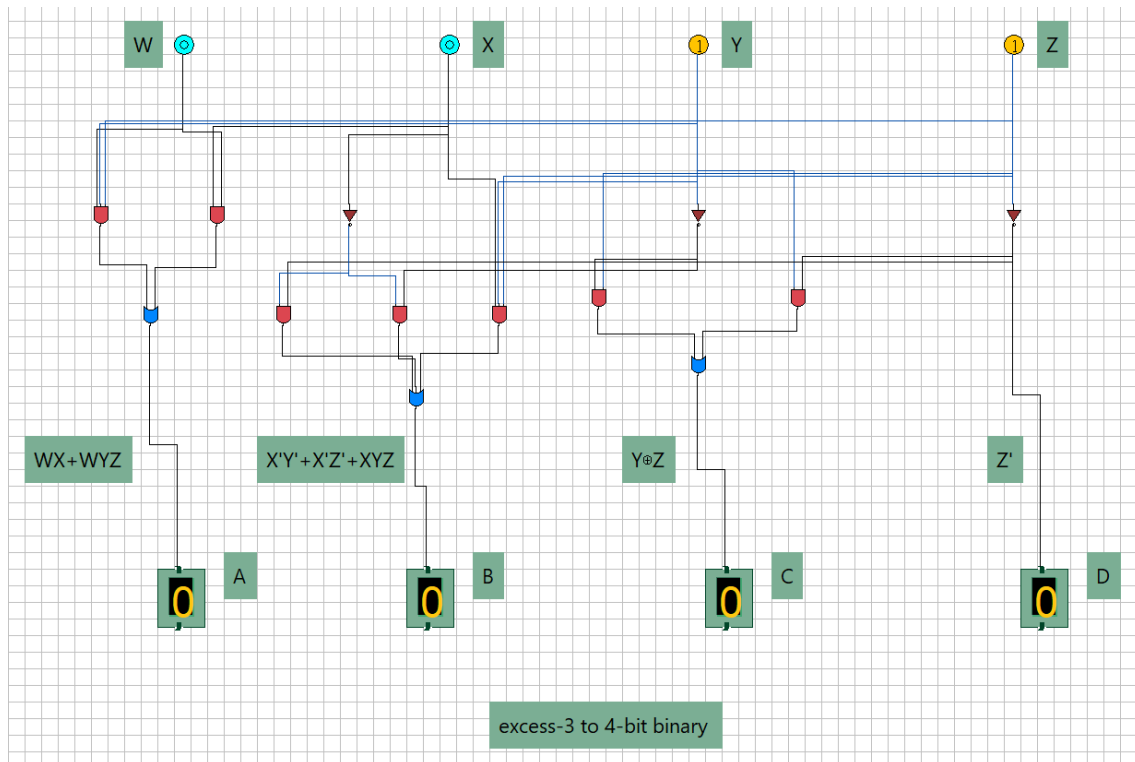

—: THE END :—